


Lec 2

(1) Laws of Resistance \rightarrow It depends upon following factors

$$R = \rho \frac{l}{a}$$

- directly prop. to the length
- Inversely prop. to area of Cross Section
- Nature of material
- Temp. of wire (Cond.)

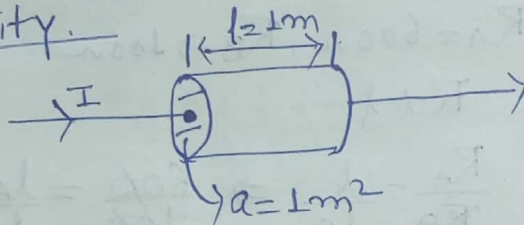Here ρ is a Constant, depending on nature of material of Conductor called as Specific Resistance or Resistivity.



$$R = \rho$$

Hence, the resistance offered by one metre length of wire, having an area of Cross-section of one square metre called Resistivity of material

$$\text{Unit } \rho = \frac{R a}{l} \Rightarrow \frac{\text{ohm} \times \text{m}^2}{\text{m}} \rightarrow \text{ohm-m}$$

• Conductance \rightarrow denoted by (G)

$$G = \frac{1}{R} = \frac{a}{\rho l} = \sigma \frac{a}{l}$$

$$\text{Unit } (G) \text{ mho}$$

Conductivity / Specific Conductance \rightarrow Basically it is property of material due to which it allows the current to flow through it.

$$\sigma = G \frac{l}{a} = \frac{\text{mho} \times \text{m}}{\text{m}^2} \Rightarrow \boxed{\text{mho/m}} \leftarrow \text{SI Unit}$$

(Q) The wire A and B of same material, but of different length L and $2L$, have radius r and $2r$,
Then Ratio of specific resistance (Cb)

- (a) 1:4 (b) 1:1
(c) 1:8 (d) 1:2

$$R = \frac{\rho l}{a} \quad \rho = \frac{Ra}{l} \Rightarrow \frac{\rho}{l}$$

(Q) Two wire A and B have same cross section are made of same material. $R_A = 600\Omega$, $R_B \rightarrow 100\Omega$. The no. of time A is longer than B

Given. $R_A = 600\Omega$, $R_B \rightarrow 100\Omega$

$R \propto l$

$$\frac{R_A}{R_B} = \frac{l_A}{l_B} \Rightarrow \frac{600}{100} = \frac{l_A}{l_B}$$

$$l_A = 6l_B$$

(Q) Find the resistivity of a material ($\Omega\text{-cm}$) of wire, whose resistance is 5Ω . Length of wire is 15m , diameter of wire is 0.15cm

Sol. Given $\rightarrow R \rightarrow 5\Omega$

$$L \rightarrow 15\text{m} \rightarrow 1500\text{cm}$$


$$A \rightarrow \pi r^2 \Rightarrow \pi \times \left(\frac{0.15}{2}\right)^2$$

$$R = \frac{\rho l}{a} = 5$$

$$\rho = \frac{Ra}{l}$$

$$\Rightarrow 5.87 \times 10^{-5} \Omega\text{-cm}$$

Ohm's law

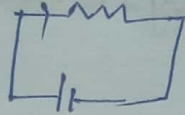

At Const. temp I flowing b/w any two pt. of Conductor (wire) is directly prop. to potential diff across them

$$\frac{V}{I} \propto R \quad \text{or} \quad I \propto V$$

But experimentally we have observed, the resistance of metallic Conductor vary with temp.

$$R_{T_2} = R_{T_1} [1 + \alpha \Delta T]$$

$$\Delta T \rightarrow T_2 - T_1$$

$R_{T_1} \rightarrow$ Resistance at temp T_1

$R_{T_2} \rightarrow$ " " " temp T_2

$\alpha \leftarrow$ Tem. Coefficient of Resistance

(Q) At 20 degree Celsius, aluminium wire has resistance of 30 Ω . The temp. Coefficient of resistance is 0.00305 per degree Celsius. What is approx. resistance of wire (Ω) at 30 degree Celsius

$$R_{T_2} = R_{T_1} [1 + \alpha \Delta T]$$

$$R_{T_1} \rightarrow 30 \Omega$$

$$\alpha \rightarrow 0.00305$$

$$\Delta T = T_2 - T_1$$

$$\Rightarrow 30 - 20$$

$$\Rightarrow 30 [1 + 0.00305 (10)]$$

$$\Rightarrow 31 \Omega$$


(Q) Find the value of temp. coeff. of resistance

We know

$$R_{T_2} = R_{T_1} [1 + \alpha \Delta T]$$

$$R_1 \rightarrow 30 \Omega, T_1 \rightarrow 0^\circ \text{C}$$
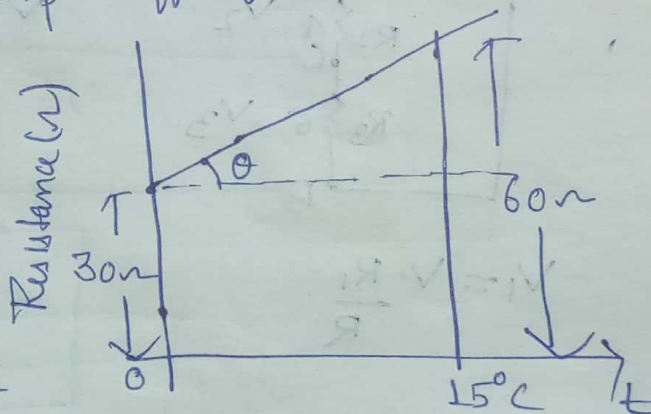
$$R_2 \rightarrow 60 \Omega, T_2 \rightarrow 15^\circ \text{C}$$



$$60 = 30 [1 + \alpha (15)]$$

$$2 = 1 + \alpha (15)$$

$$\alpha \Rightarrow \frac{1}{15} \Rightarrow 0.066\bar{6} (^\circ \text{C})$$


(2) Resistance in Series

- (a) Same Current through all Conductor
- (b) Voltage drop is different
- (c) Sum of three voltage drop is equal to voltage applied across the three Conductor.
- (d) Resistance are additive


Resistance in Parallel

- (a) P.d same
- (b) Current different
- (c) I
- (d) Conductance are additive

Voltage division Rule

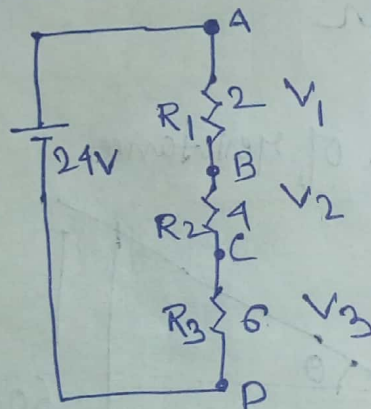

$$V_1 = V \cdot \frac{R_1}{R}$$

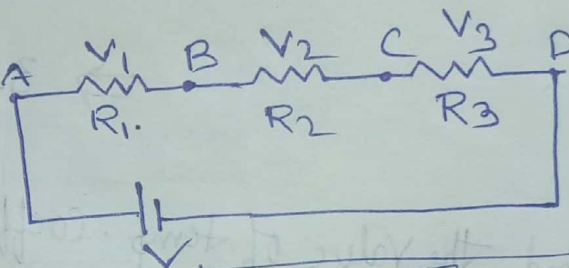


$$V_1 = V \cdot \frac{R_1}{R_{Total}}$$

$$V_2$$

$$V_3$$


Current division Rule

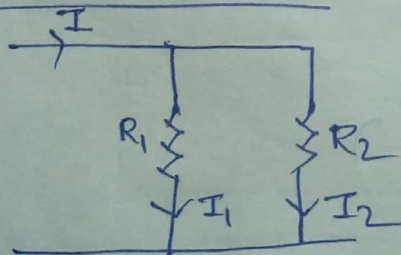

$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$I_1 = \frac{I}{R_1 + R_2} \cdot R_2$$

(i)

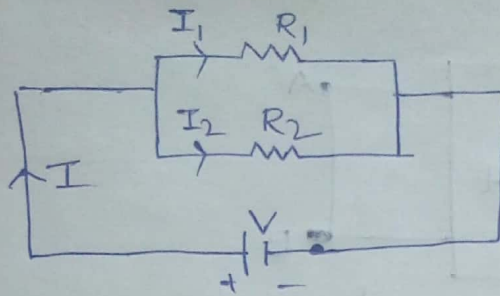

$$V = I_1 R_1 = I_2 R_2$$

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$

\therefore From this we observe branch of parallel ckt is inversely prop. to resistance,

$$V = I_1 R_1 = I_2 R_2 = IR$$


$$\text{ER}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 R_1 = IR = I \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = I \frac{R_2}{R_1 + R_2}$$

*

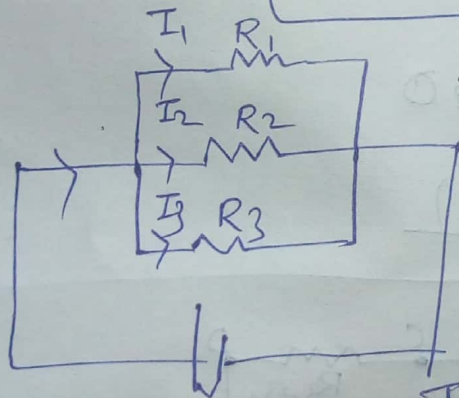


$$I_1 R_1 = I_2 R_2 = I_3 R_3 = IR = V$$

$$R_{eq} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$I_1 R_1 = IR = I \times \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$I_1 = I \times \frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

(3) Short ckt. →

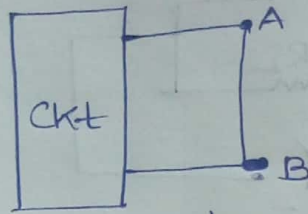

When two ^{terminal} are connected by thick metallic wire then, there will be short ckt


$$R=0$$

$$V \rightarrow ?$$

$$V = I \times 0 \Rightarrow 0$$

Current will be very large (∞)

Open ckt.

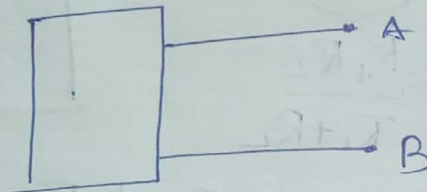


When two terminal ~~are~~ have no direct connection b/w them.

$$R \rightarrow \infty$$

$$\Rightarrow I \rightarrow 0$$

$$V(\infty)$$

(Q)

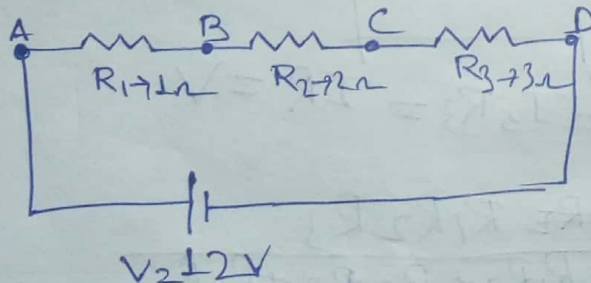

$$V \rightarrow 12, R_{eq} \rightarrow 6\Omega, I \rightarrow \frac{12}{6} \Rightarrow 2A$$

$$P = I^2 R \Rightarrow 2^2 \times 6 = 24W$$

Now, CD is short ckt

$$R_{eq} = 3\Omega$$

$$I = \frac{12}{3} \rightarrow 4A$$

$$P \rightarrow I^2 R_{eq}$$


$$P \Rightarrow 16 \times 3 \\ = 48W$$

* Power is rate of change of energy

$$P = \frac{dw}{dt}$$

$$= \frac{dV}{dq} \cdot \frac{dq}{dt}$$

$$P = V(t) \cdot i(t)$$

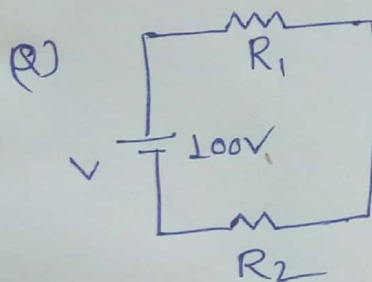

→ If ckt is open

$$R \rightarrow \infty$$

$$I \rightarrow 0$$

then there will be no voltage drop

