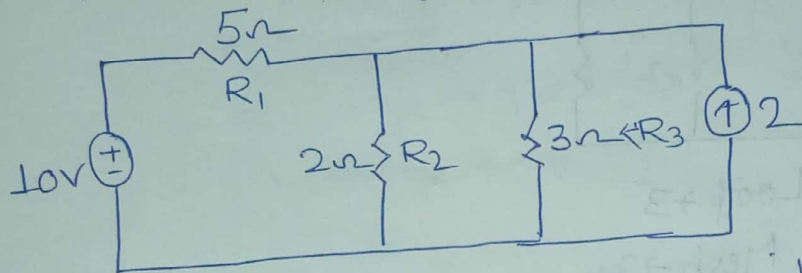


Lec. 04


Circuit → A circuit is closed Conducting path through which an electric Current flows

Branch → A branch is Single element or Component in ckt.




5; Branch → 10V, 2A, Three resistor → R_1, R_2, R_3

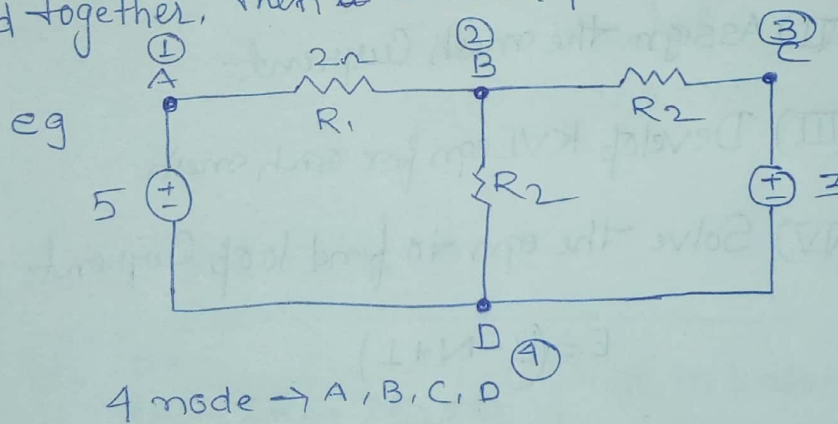
Node → When two or more than two element are Connected together, then ~~is~~ common pt is called node



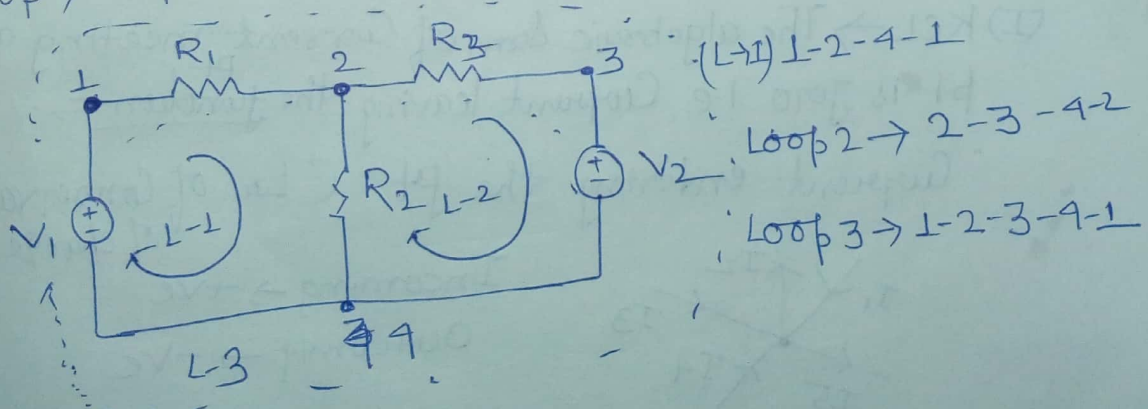Loop → Any closed path in electrical ckt is called loop



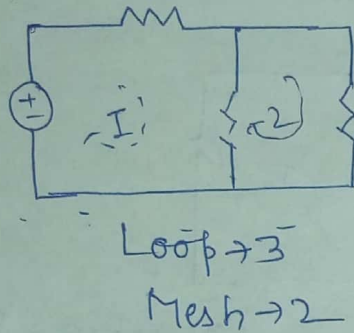Mesh \rightarrow A closed path in the Circuit which does not enclose any other closed path inside it. It is applicable for only planar network. Planar n/w is the one that can be drawn in plane with no-branch crossing one another




Procedure for applying Mesh analysis

- (I) Identify total no. of mesh
- (II) Assign the mesh current
- (III) Develop KVL eqn for each mesh
- (IV) Solve the eqn to find loop current

$$E = (B - N + 1)$$

(2) Kirchhoff's law

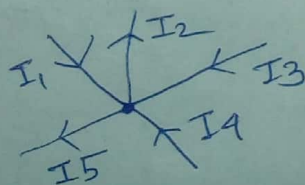(I) KCL \rightarrow The algebraic sum of current meeting at pt is zero i.e. Current leaving the ^{pt} ~~function~~
 Current entering the pt. (Law of Conservation of charge)




Incoming $\rightarrow +ve$
Outgoing $\rightarrow -ve$

$$I_1 + (-I_2) + I_3 + (-I_4) + I_5 = 0$$


$$I_1 + I_3 + I_5 = I_2 + I_4$$

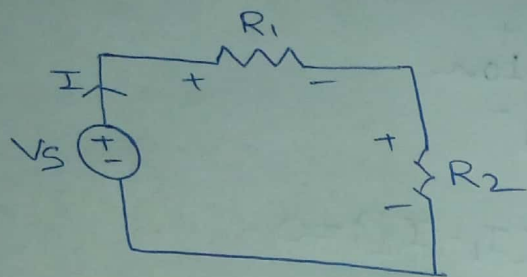KVL \rightarrow Algebraic sum of all the voltage in closed loops zero. Based on Law of Conservation of energy




Rise in voltage \rightarrow +ve Sign

Fall in voltage \rightarrow -ve Sign

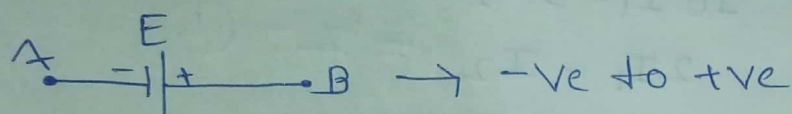

Rise in potential

$V \rightarrow$ +ve Sign.

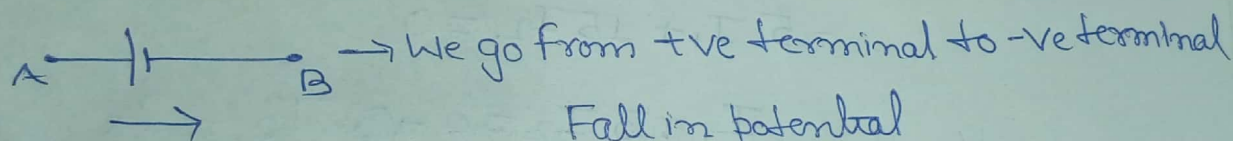

Fall in potential

$V \rightarrow$ -ve.

or

$$+V_S - IR_1 - IR_2 = 0$$


or

$$-V_S + IR_1 + IR_2 = 0$$

Rise in potential
 \Rightarrow -ve

Drop in poten. \rightarrow +ve

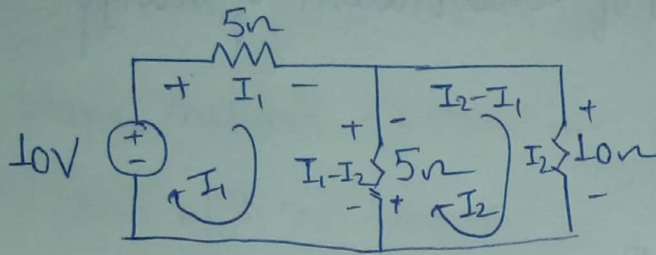(Q) Find power loss in 10Ω resistor using mesh analysis



$$\text{Loop 1} \rightarrow -10 + 5I_1 + 5(I_1 - I_2) = 0$$

$$-10 + 5I_1 + 5I_1 - 5I_2 = 0$$

$$10I_1 - 5I_2 = 10$$

$$2I_1 - I_2 = 2 \quad \text{--- (1)}$$

$$\text{L.2} \quad 10I_2 + 5(I_2 - I_1) = 0$$

$$-5I_1 + 15I_2 = 0$$


$$-I_1 + 3I_2 = 0 \rightarrow \text{--- (2)} \quad I_2 = \frac{2}{5}$$

$$I_2 = I_2^2 \times 10$$

$$= \left(\frac{2}{5}\right)^2 \times 10$$

$$P_{10} = \frac{8}{5} \text{ W}$$

Classification of electric network

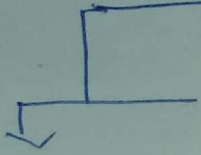

Active n/w \rightarrow A ckt. which contain at least one energy source
Voltage or Current source \rightarrow that capable of providing power gain.

Passive n/w \rightarrow Only passive element, no energy source

Linear n/w \rightarrow Parameter always constant w.r.t time
(homogeneity and additive)

Non-linear n/w \rightarrow

Bilateral \rightarrow Ind. of direction of current

Unilateral \rightarrow dep on direction of current

Lumped \rightarrow physically separable (separate element)
Small in size

distributed \rightarrow not physically separable

Note \rightarrow Linear element will exhibit bidirectional