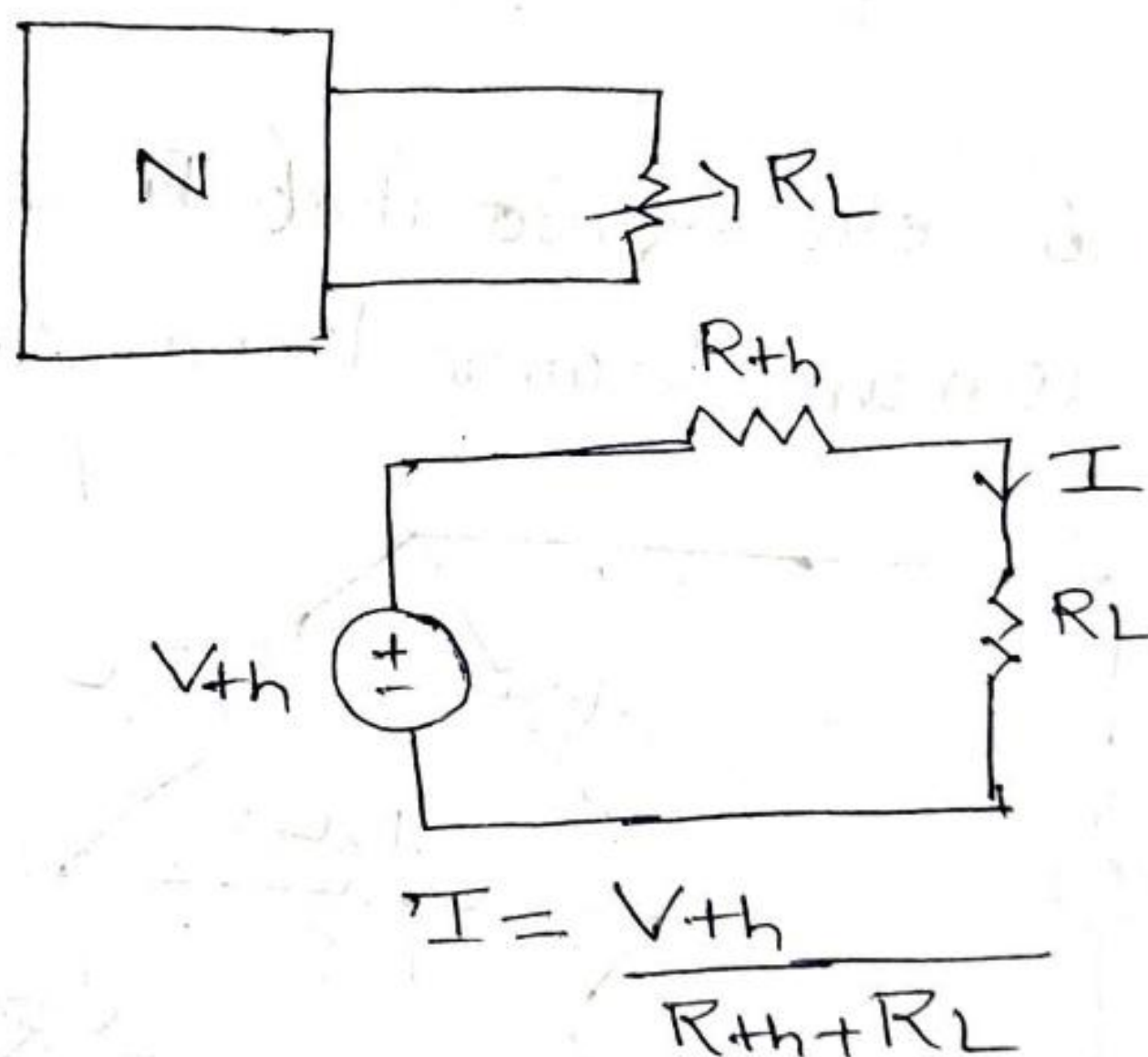


## Maximum Power Transfer Theorem.

The output obtained from a network is maximum when load resistance is equal to internal resistance of the network as seen from the load.

According to Thevenin theorem, every network can be represented ~~by~~ <sup>having</sup> single voltage source having effective internal resistance  $R_{th}$  shown in Fig.



Output power,  $P = I^2 R_L$

$$P = \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$

Power will be maximum  $\frac{dP}{dR_L} = 0$

$$\frac{dP}{dR_L} = V_{th}^2 \left[ \frac{(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L)}{(R_{th} + R_L)^2} \right] = 0$$

$$R_{th} + R_L - 2R_L = 0$$


$$R_{th} - R_L = 0$$



$$P_{\max} = \frac{V_{Th}^2}{(R_{Th} + R_{Th})^2} \cdot R_{Th}$$



$$= \frac{V_{Th}^2}{4R_{Th}^2} \cdot R_{Th}$$

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$

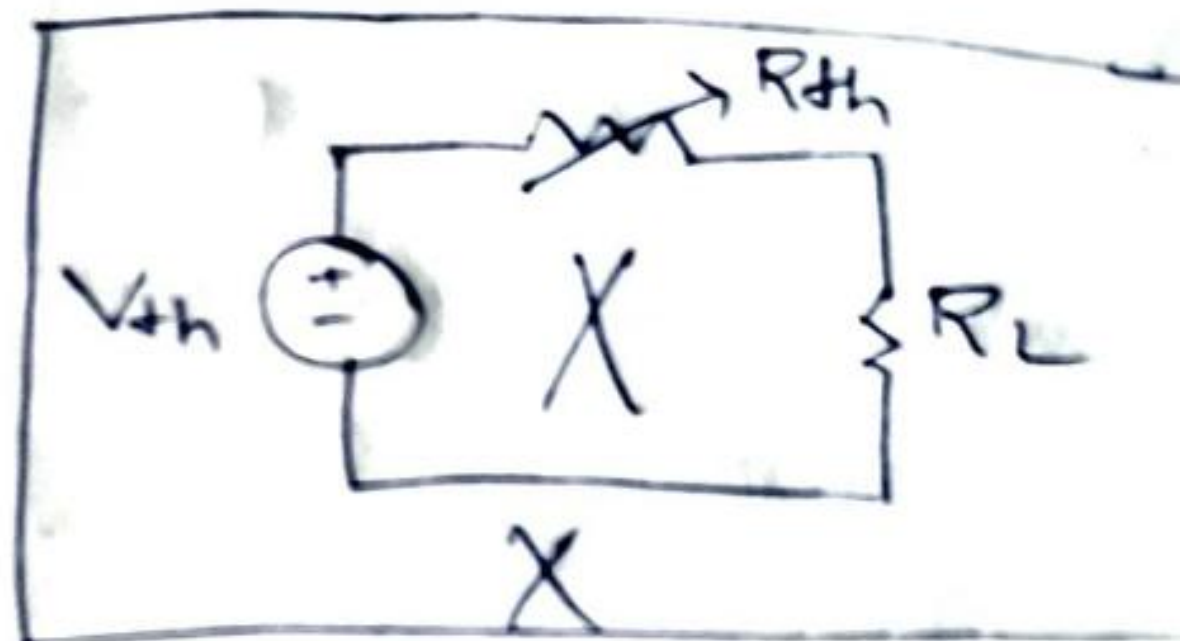


∴ Thus for maximum power transfer, load resistance  $R_L$  is made equal to internal resistance of the Source  $R_{Th}$ .

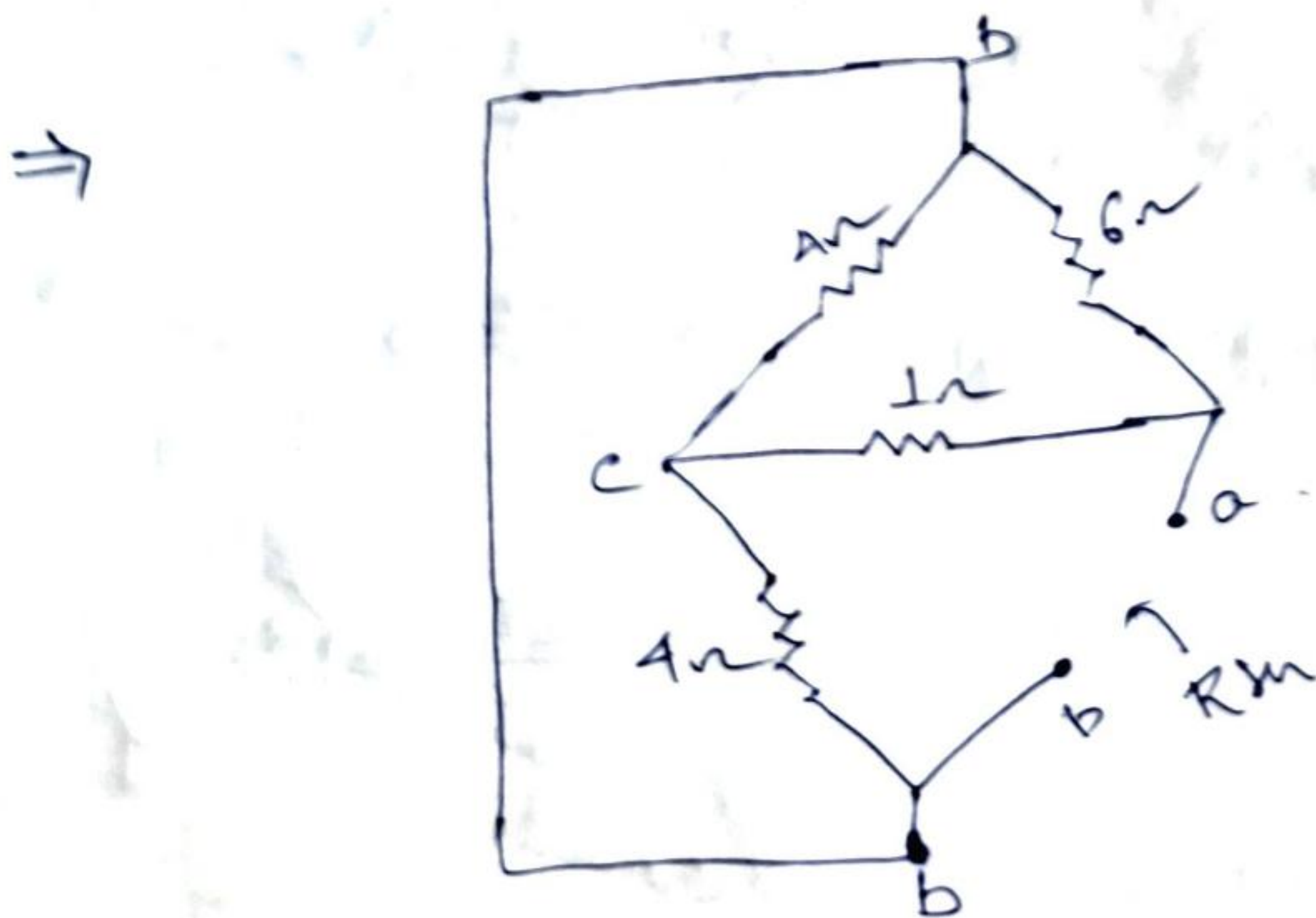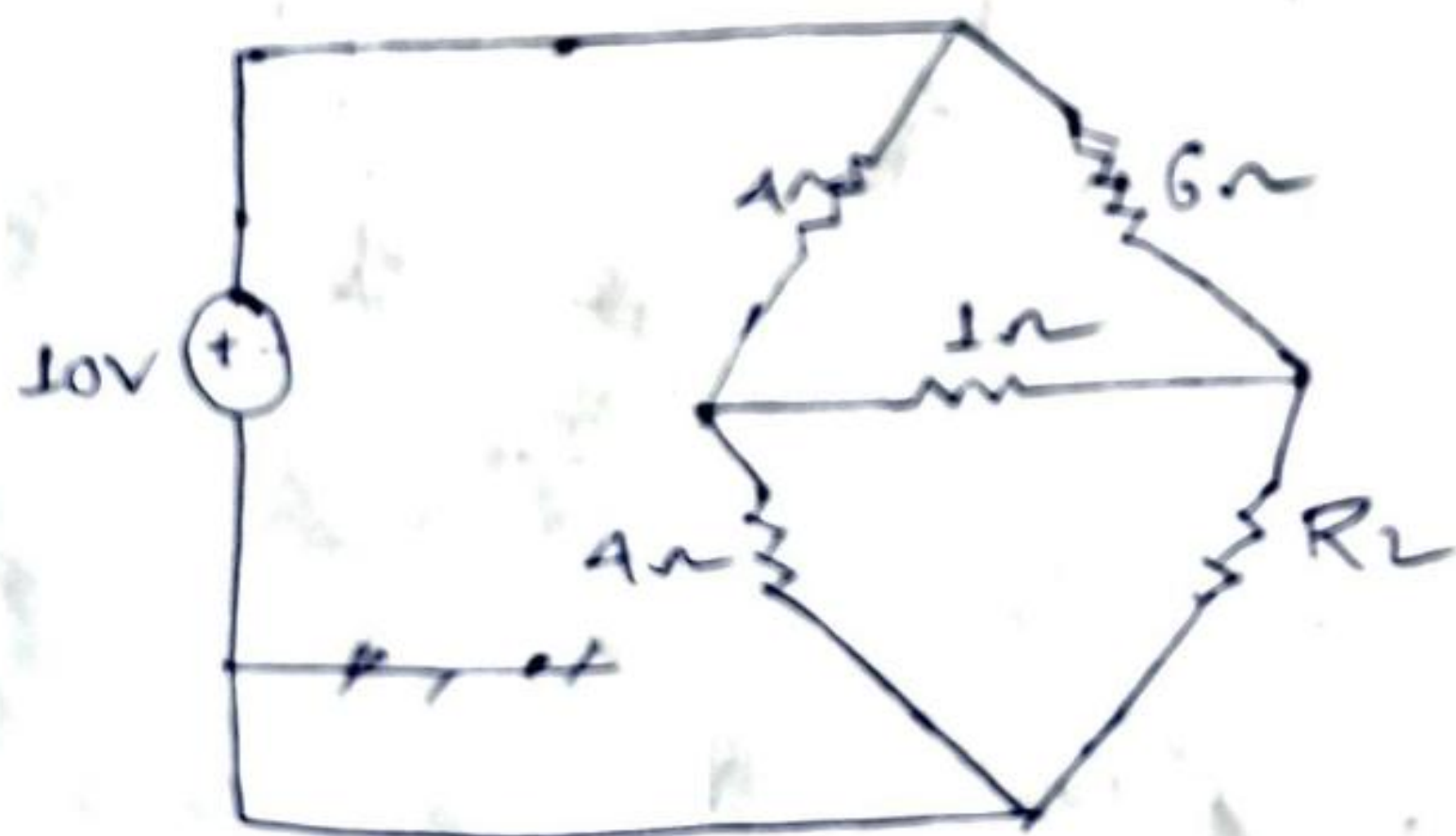(Q) In the below network, so that Find Value of  $R_L$  so that maximum power transfer from it.





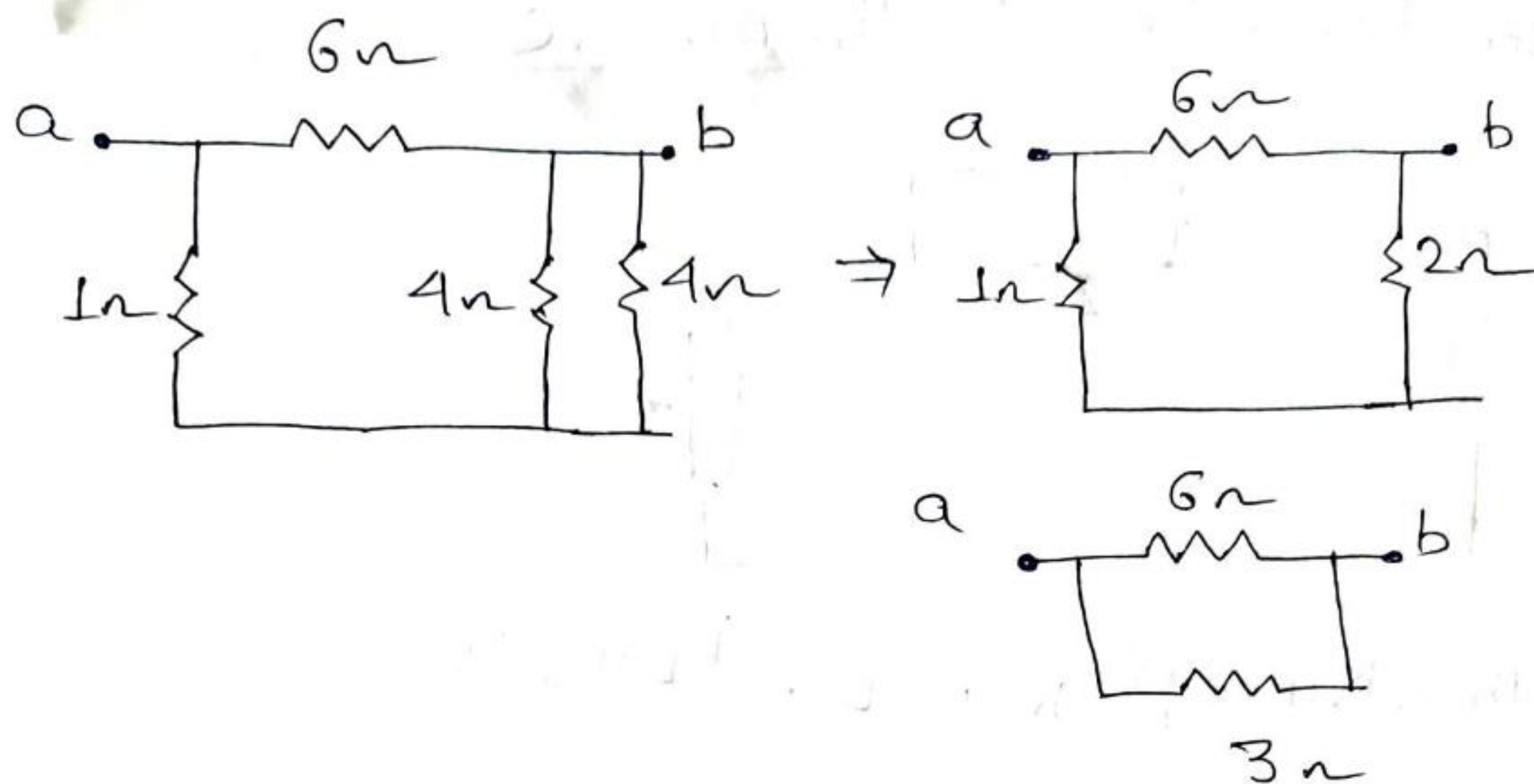

$$R_{ab} \Rightarrow 6 \parallel 3$$


$$\Rightarrow 2$$

$$R_{th} = R_{ab} = 2\Omega$$

For maximum power,  $R_L = R_{th}$ .

$$(2\Omega)$$

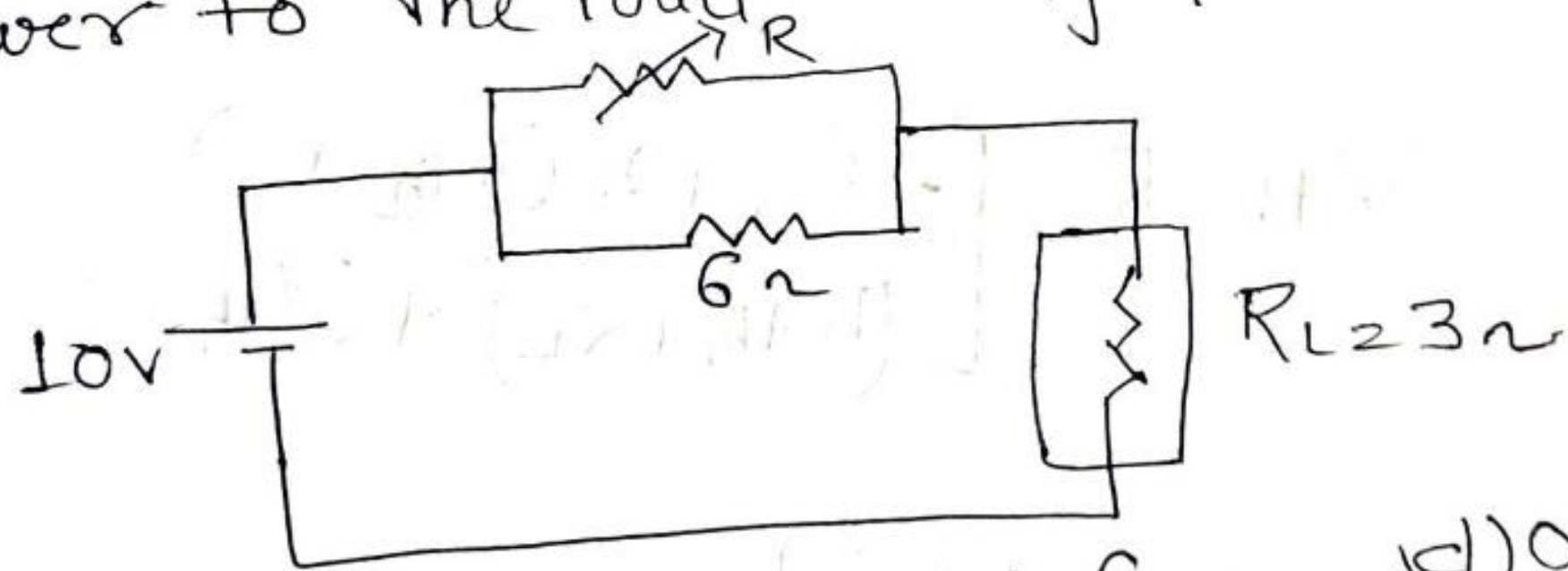Q) Find the value of  $R$  required for the transfer of maximum power to the load having resistance of  $3\Omega$ .




(a) 0      (b)  $3\Omega$       (c)  $6\Omega$       (d)  $\infty$

$$I = \frac{V_{th}}{R_{th} + R_L}$$

$$P = I^2 R_L$$

$R$	$6 \parallel R$	$I = \frac{10}{6 \parallel R + 3}$	$P_{3\Omega} = I^2 \times 3$
0	0	$\frac{10}{3}$	33.3W.
3	2	$\frac{10}{5} = 2$	12W
6	3	$\frac{10}{6}$	8.33.



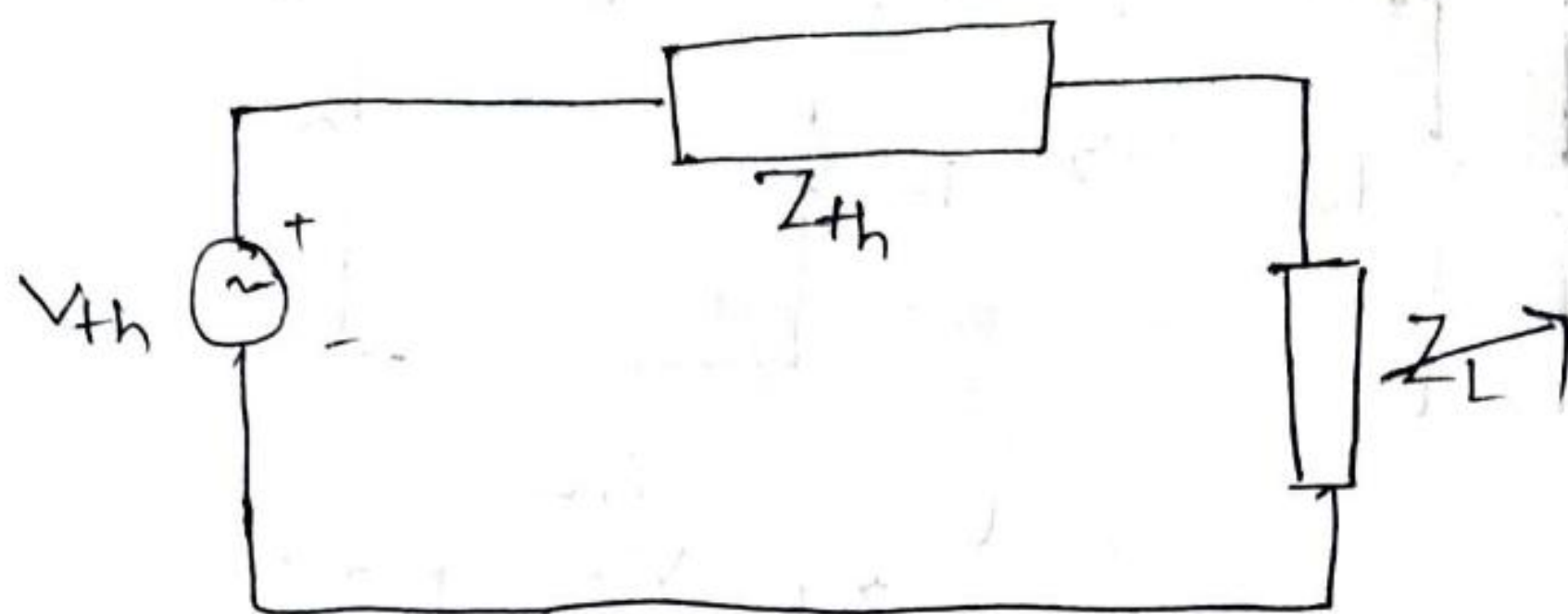

$$Z_{th} = R_{th} + jX_{th}, Z_L = R_L + jX_L$$

$$I = \frac{V_{th}}{Z_{th} + Z_L}$$

$$|I| = \frac{V_{th}}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}}$$

$$P = |I|^2 R_L$$

$$P = \frac{V_{th}^2 \cdot R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$


$$\frac{dP}{dX_L} = V_{th}^2 R_L \left[ \frac{-[0 + 2(X_{th} + X_L)]}{[(R_{th} + R_L)^2 + (X_{th} + X_L)^2]^2} \right] = 0$$

$$Z_L = Z_{th}^*$$

∴ It will deliver maximum power to Variable Complex load. When load impedance is equal to Complex of Source impedance.



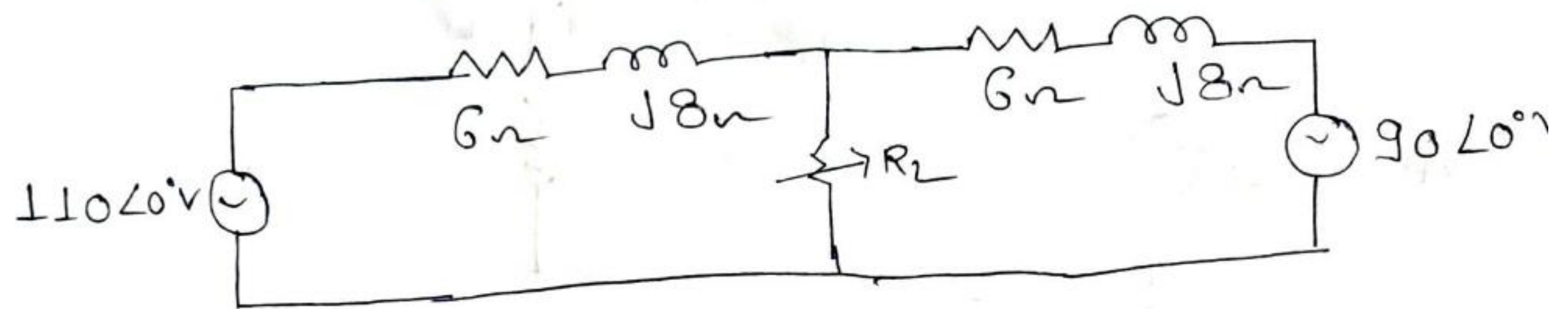
(Q) Find the maximum power, dissipation in load resistance



Objective -  $P_{\max} = |I_L|^2 R_L$

$$I_L = \frac{V_{th}}{Z_{th}}$$


(i) Calculu. of  $Z_{th}$

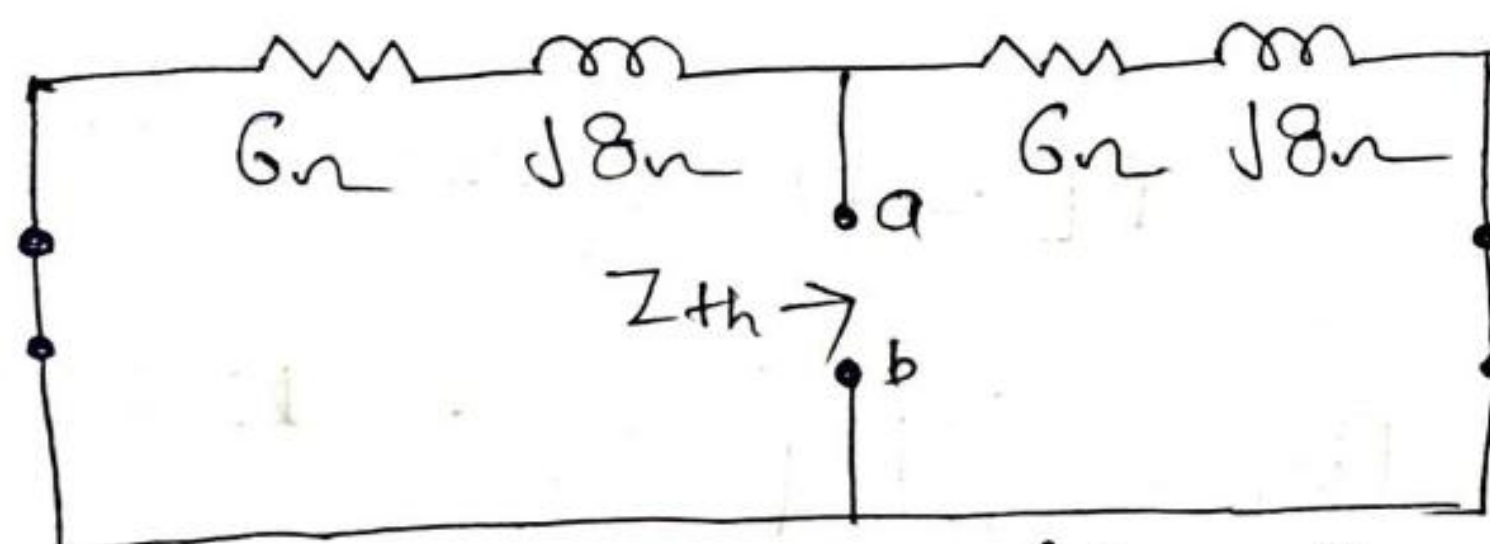

$$Z_{th} = (6 + j8) \parallel (6 + j8)$$


$$Z_{th} = (3 + j4) \Omega$$

(ii) Calculation of  $V_{th}$

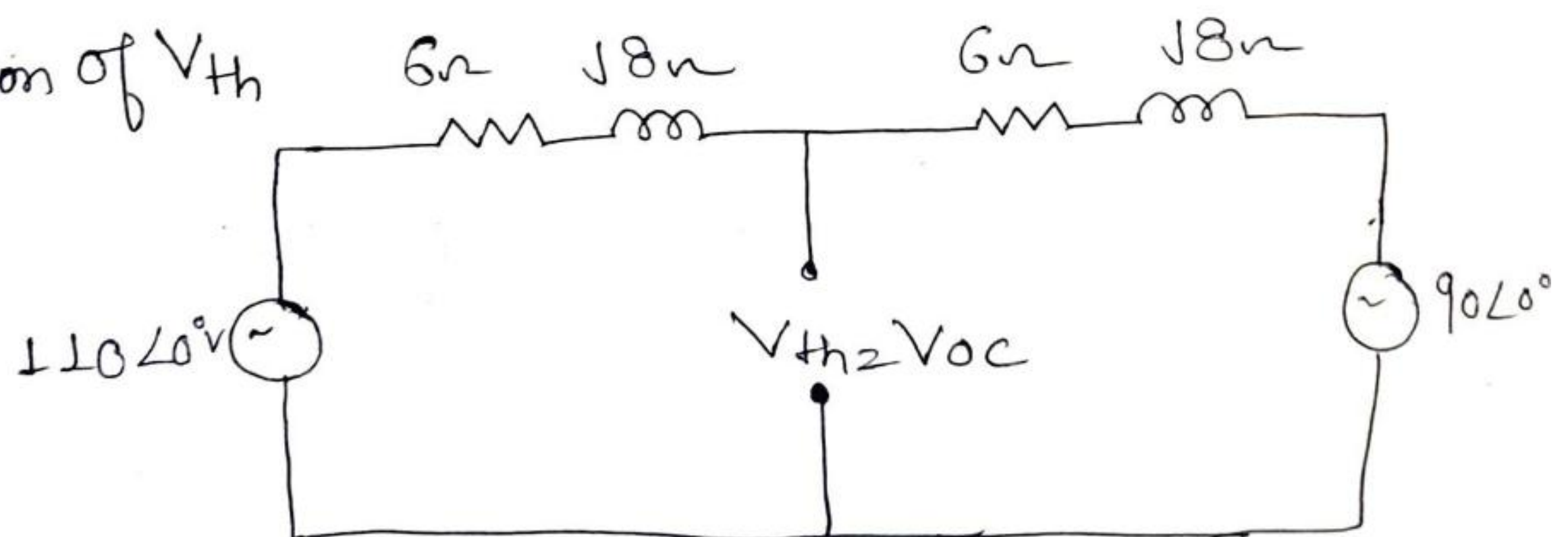

$$\frac{V_{th} - 110 \angle 0^\circ}{6 + j8} + \frac{V_{th} - 90 \angle 0^\circ}{6 + j8} = 0$$

$$V_{th} = 100 \angle 0^\circ$$

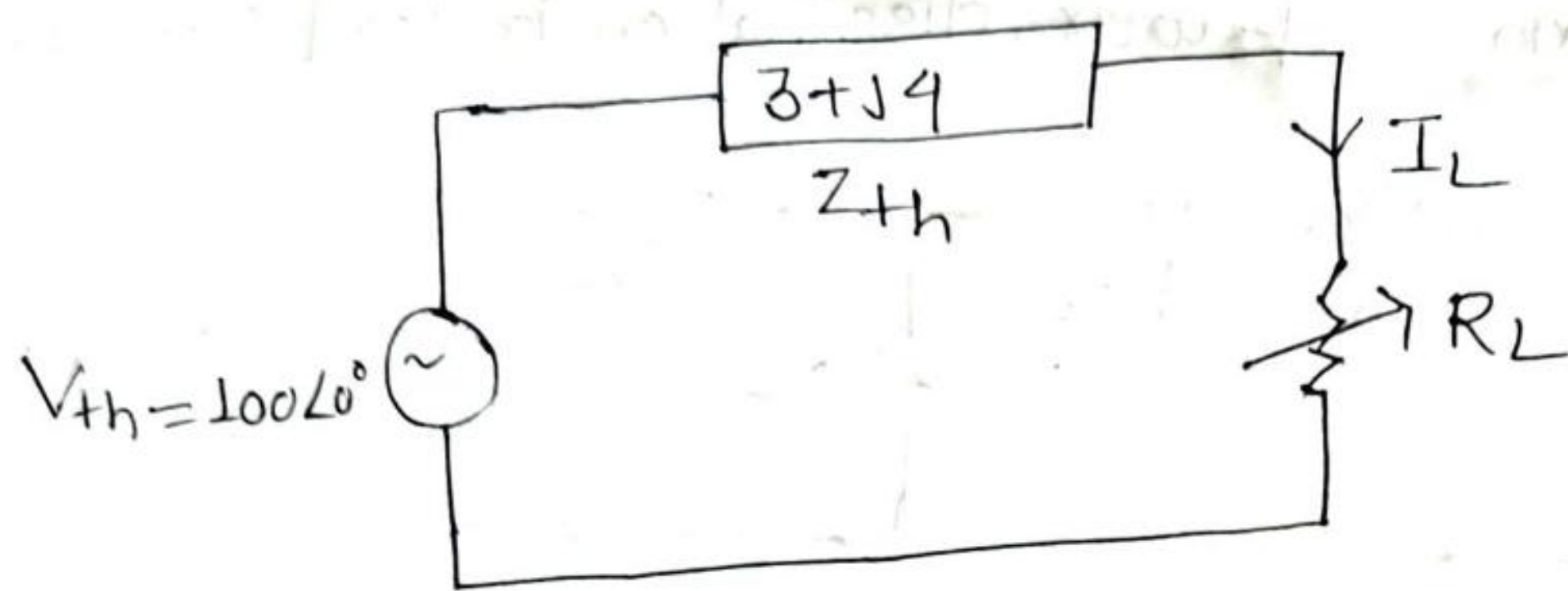

Maxm. power transfered to Load.

$$R_L = |Z_{th}| = \sqrt{3^2 + 4^2} = 5\Omega$$

$$I_L = \frac{V_{th}}{3 + j4 + 5} = \frac{100}{8 + j4}$$

$$I_L = 11.18 \angle -26.56^\circ$$

$$P_{RL} = |I_L|^2 R_L = 11.18^2 \times 5 = 625W$$



$Z_S$	$Z_L$	Condition for MPT	$P_L$ (maxm. power transfer to load)
$R_S + j0$	<del><math>R_L + j0</math></del>	$R_L = R_S$	$ I ^2 R_L = \frac{V_S^2}{4R}$
$R_S + jX_S$	<del><math>R_L + jX_L</math></del>	$R_L = \sqrt{R_S^2 + (X_S + X_L)^2}$	$ I ^2 R_L$
$R_S + jX_S$	<del><math>R_L + jX_L</math></del>	$X_L + X_S = 0$	$ I ^2 R_L = \frac{V_S^2 R_L}{R_S + R_L}$
$R_S + jX_S$	<del><math>R_L + jX_L</math></del>	$Z_L = Z_S^*$	$ I ^2 R_L = \frac{V_S^2}{4R_S}$
$R_S + jX_S$	<del><math>R_L + j0</math></del>	$R_L = \sqrt{R_S^2 + X_S^2}$	$ I ^2 R_L$
$R_S + j0$	<del><math>R_L + jX_L</math></del>	$R_L = \sqrt{R_S^2 + X_L^2}$	$ I ^2 R_L$