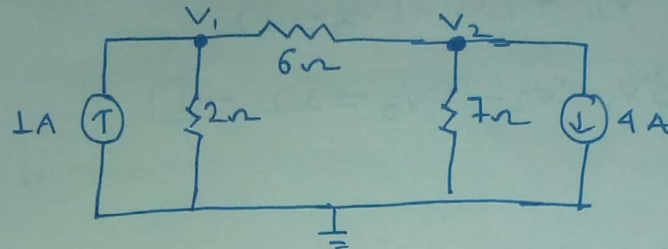


(Q) Determine node voltage in the ckt



Apply KCL at node-1

$$\frac{V_1}{2} + \frac{V_1 - V_2}{6} - 1 = 0$$

$$0.667V_1 + 0.167V_2 = 1$$


Apply KCL at node-2

$$\frac{V_2 - V_1}{6} + \frac{V_2}{7} + 4 = 0$$

$$-0.167V_1 + 0.309V_2 = -4$$

$$V_1 = -2V, V_2 = -14V$$

(Q) Determine Voltage at nodes

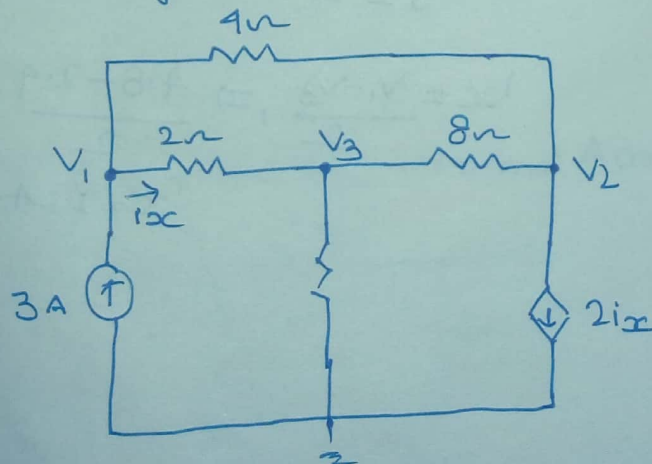

$$i_x = \frac{V_1 - V_3}{2}$$

Apply KCL at node 1,

$$\frac{V_1 - V_2}{4} + \frac{V_1 - V_3}{2} = 3$$

$$V_1 - V_2 + 2V_1 - 2V_3 = 12$$

$$3V_1 - V_2 - 2V_3 = 12 \quad \text{--- (1)}$$

Apply KCL at node 2,

$$\frac{V_2 - V_1}{4} + \frac{V_2 - V_3}{8} + 2i_x = 0$$

$$6V_1 + 3V_2 - 9V_3 = 0 \quad \text{--- (2)}$$

Apply KCL at node 3,

$$\frac{V_3 - V_1}{4} + \frac{V_3 - V_2}{8} + \frac{V_3}{2} = 0$$

$$-4V_1 - V_2 + 7V_3 = 0$$

$$V_1 = 4.8 \text{ V}$$



$$V_2 = -2.4 \text{ V}$$

$$V_3 = 2.4 \text{ V}$$

$$i_x = \frac{V_1 - V_3}{2} \Rightarrow \frac{4.8 - 2.4}{2}$$


$$i_x = 1.2 \text{ A}$$

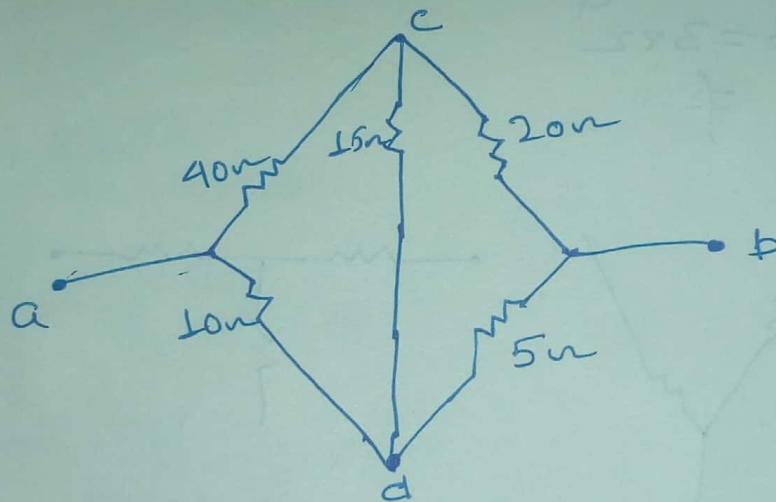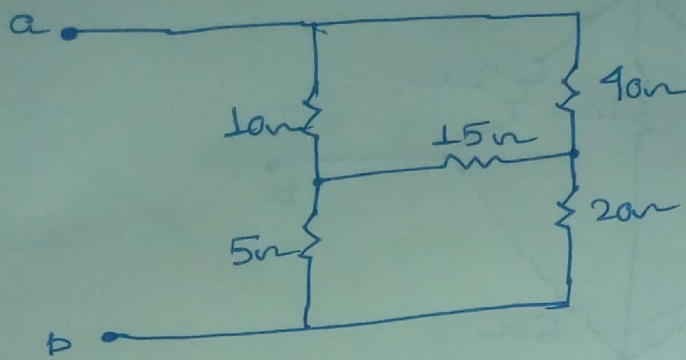(Q) Find equivalent resistance b/w terminal A and B?



$$V_c = V_d = 0$$


$$I_{cd} = 0$$

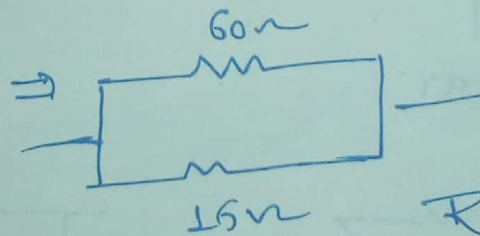


$$R_{eq} = \frac{60 \times 15}{60 + 15}$$

$$= 12\Omega$$

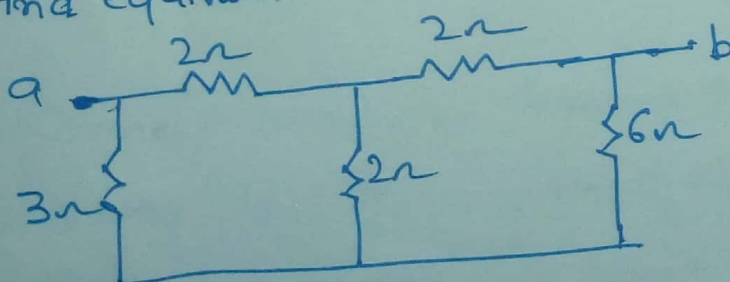
(Q) Find equivalent resistance b/w terminal A and B?



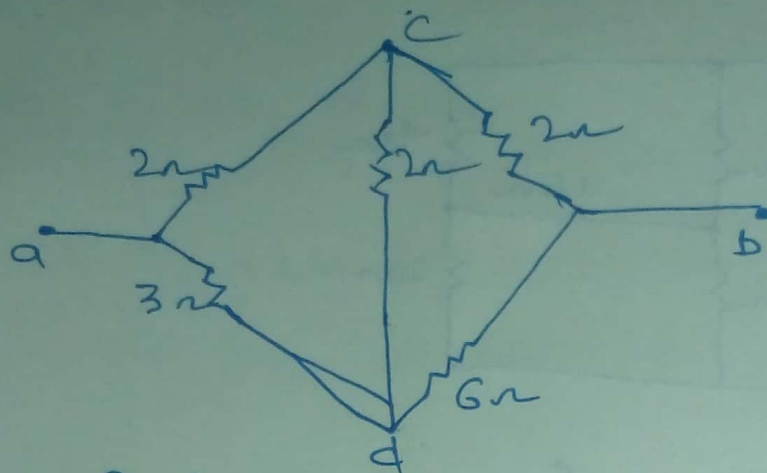

$$2 \times 6 = 3 \times 2$$


$$\neq$$

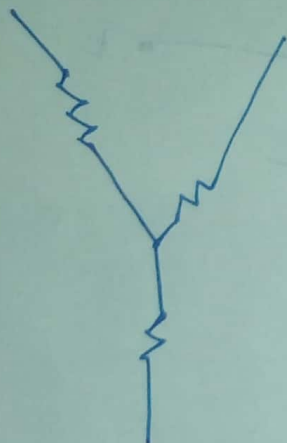


Star




T-N/W

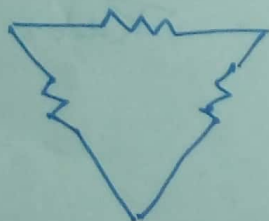

Delta

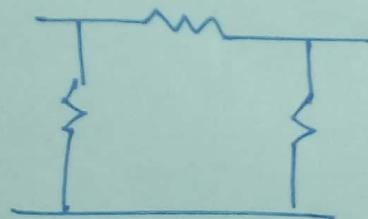

π-N/W

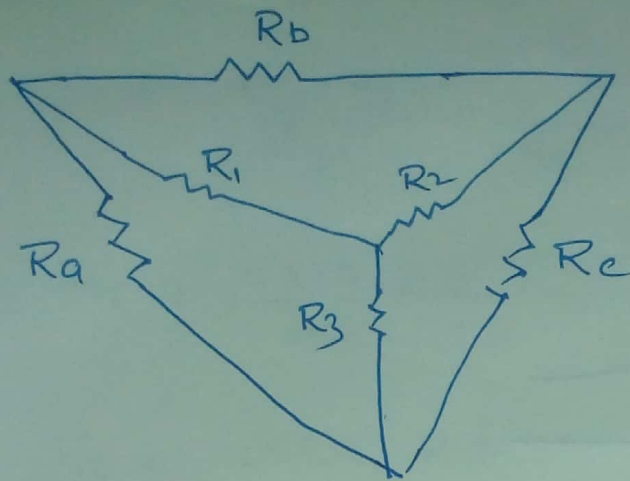

$\Delta \rightarrow Y$ (Delta to Star)

$$R_1 = \frac{R_a \cdot R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_b \cdot R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a \cdot R_c}{R_a + R_b + R_c}$$


$Y \rightarrow \Delta$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


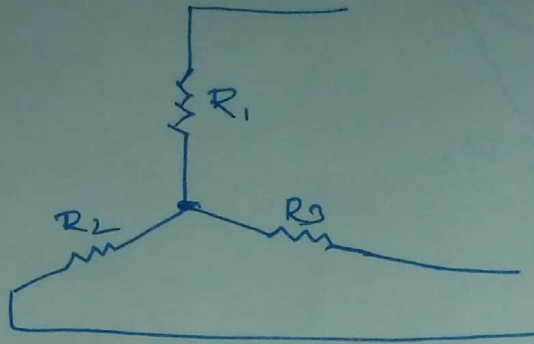
Star Connection \rightarrow When elements are connected in such a way that finishing end of all the elements are connected to common point or star pt or neutral pt. is said to be star connection.



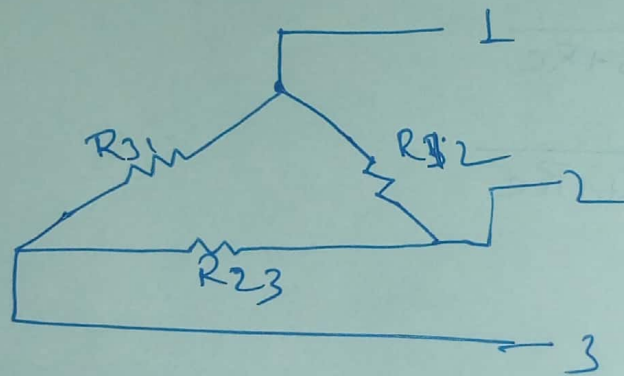Delta Connection → element are Connected in such a way finishing end of first element Connected to starting end of second element



(Q) Convert Δ into Y

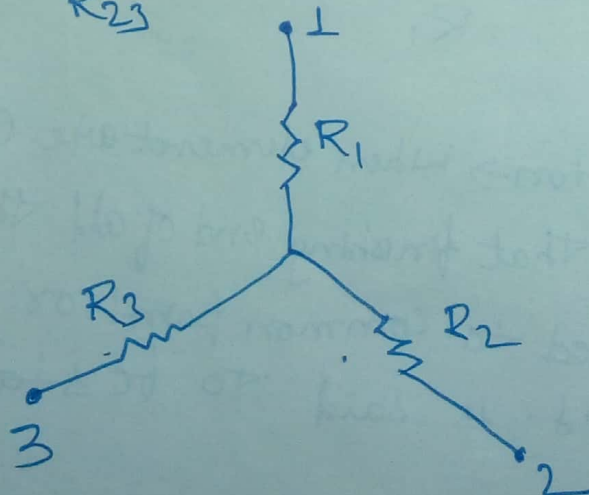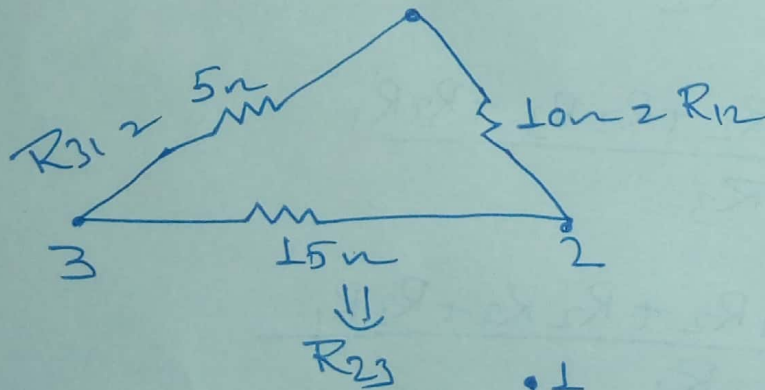


$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 \Rightarrow \frac{5 \times 10}{30} = \frac{5}{3}$$

$$R_2 = \frac{10 \times 15}{30} \Rightarrow 5 \Omega$$

$$R_3 = \frac{5 \times 15}{30} = \frac{5}{2} \Omega$$

(Q) Convert Y into Δ .

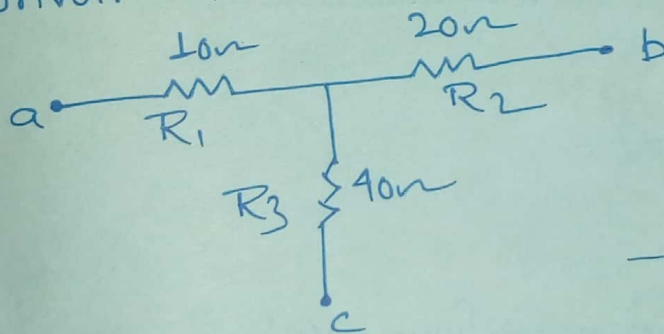

$$R_{ab} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

or

$$R_{ab} = \frac{R_3 R_1 + R_2 R_3 + R_1 R_2}{R_3}$$

$$10 + 20 + \frac{10 \times 20}{40}$$

$$R_{ab} = 35 \Omega$$

$$R_{bc} = R_2 + R_3 + \frac{R_2 \cdot R_3}{R_1}$$

$$= 20 + 40 + \frac{20 \times 40}{10}$$